

SISTEM DIGITAL (TIF-1106)

Pertemuan 3: Gerbang Logika Dasar/Komposit, IC TTL 74xx, & Timing Diagram

Capaian Pembelajaran Pertemuan 3

Sub-CPMK 3

Mahasiswa mampu menganalisis karakteristik gerbang logika dasar (AND, OR, NOT) dan komposit (NAND, NOR, XOR, XNOR), mengidentifikasi pinout IC seri TTL 74xx, serta membaca diagram pewaktuan (*timing diagram*).

Simbol ANSI/IEEE Gerbang Logika Utama



AND (7408)



OR (7432)



NAND (7400)



XOR (7486)

Sirkuit Kombinasi Gerbang Logika

